

B.TECH DEGREE EXAMINATION, JANUARY 2023

THIRD SEMESTER

INFORMATION TECHNOLOGY

DIGITAL SYSTEM DESIGN

PART-A (10X2=20 MARKS)

1. Write 16-bit 2's complement representation for the decimal number -28.

16-bit representation of decimal number +28 is : $(0000\ 0000\ 0001\ 1100)_2$.

-28 is nothing but 2's complement of +28.


1's complement of +28: $1111\ 1111\ 1110\ 0011$

2's complement :
$$\begin{array}{r} 1111\ 1111\ 1110\ 0011 \\ +1 \\ \hline 1111\ 1111\ 1110\ 0100 \end{array}$$

2's complement of -28 is : $1111\ 1111\ 1110\ 0100$

2. Find the minimum number of 2-input NAND gates required to implement a 2 input XOR gates and draw the logic diagram.

Solution:

 

3. A four bit ripple carry adder is realized using 4 identical full adder. The carry propagation delay of each (FA) is 13ns. Calculate the worst case delay.

Solution:

Carry propagation delay of each
FA = 13 nsec.


Sum propagation delay of each FA = 4 nsec.

So, in 4-bit ripple carry adder, worst case
delay of this 4-bit adder will be
= $(4 \times 13) \text{ nsec} + 4 \text{ nsec}$.
= 56 nsec.

4. implement the given function using multiplexer $F(A,B,C) = \sum m(0,3,4)$.

Solution:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

 

5.what is sequential circuit?How does it differ from combinational circuit?

Parameters	Combinational Circuit	Sequential Circuit
Meaning and Definition	It is a type of circuit that generates an output by relying on the input it receives at that instant, and it stays independent of time.	It is a type of circuit in which the output does not only rely on the current input. It also relies on the previous ones.
Feedback	A Combinational Circuit requires no feedback for generating the next output. It is because its output has no dependency on the time instance.	The output of a Sequential Circuit, on the other hand, relies on both- the previous feedback and the current input. So, the output generated from the previous inputs gets transferred in the form of feedback. The circuit uses it (along with inputs) for generating the next output.

6.Give the excitation table for D-FF AND T-FF.

D-FLIP FLOP

Q	Q ⁺	D
0	0	0
0	1	1
1	0	0
1	1	1

T-FLIP FLOP

Excitation table:

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0

7. List the major difference between PAL AND PLA.

S.NO	PLA	PAL
1.	PLA stands for Programmable Logic Array.	While PAL stands for Programmable Array Logic.
2.	PLA speed is lower than PAL.	While PAL's speed is higher than PLA.
3.	The complexity of PLA is high.	While PAL's complexity is less.
4.	PLA has limited amount of functions implemented.	While PAL has a huge number of functions implemented.
5.	The cost of PLA is also high.	While the cost of PAL is low.
6.	Programmable Logic Array is less available.	While Programmable Array Logic is more available than Programmable Logic Array.

8. What are the steps for the design of asynchronous sequential circuit?

1. Create a state table or state diagram from the given problem statement.
2. Create a new reduced state table by removing all the redundant states.
3. Create the transition table.
4. Write the excitation and output Boolean equations and simplify them.
5. Draw the logic diagram.

9. Define gate-level modelling?

Gate level modeling is virtually the lowest level of abstraction because the switch-level abstraction is rarely used. Gate level modeling is **used to implement the lowest-level modules in a design, such as multiplexers, full-adder, etc.** Verilog has gate primitives for all basic gates.

10. Write the syntax for even construct.

A HDL is a domain specific language, specifically designed to support the description of digital logic circuits and clock driven sequential logic. As such a HDL contains **special constructs to enable the description of digital hardware and RTL elements.**

PART-B(5X11=55 MARKS)


UNIT 1

11. Simplify the following Boolean function using K-MAP and implement using only NAND gates $F(A,B,C,D) = \sum m(1,3,4,11,12,13,14,15) + \sum d(2,5,6,7)$.

Solution:

$$F(A,B,C,D) = \sum m(1,3,4,11,12,13,14,15) + \sum d(2,5,6,7)$$


4-Variable K-map.

 

1-0001	2-0010
3-0011	5-0101
4-0100	6-0110
11-1011	7-0111
12-1100	
13-1101	
14-1110	
15-1111	

$$Y = \text{Sop} = B + CD + A'D \Rightarrow \overline{Y} = \overline{B \cdot CD \cdot A'D} \\ \text{Pos} = A' \cdot C \\ Y = \overline{\overline{B \cdot CD \cdot A'D}}$$

Logic Diagram using NAND gates.

 

OR

12. Minimize the given Boolean function using Quine McCluskey $F(A,B,C,D) = \sum m(5,7,8,9,10,11,14,15)$.

Solution:

$$F(A,B,C,D) = \sum m(5,7,8,9,10,11,14,15)$$

Step 1: Binary equivalent for decimal nos.

Decimal number	Binary equivalent
5	0101
7	0111
8	1000
9	1001
10	1010
11	1011
14	1110
15	1111

Step 2: Grouping

No. of ones	Decimal no.	Binary equivalent
1	8	1000 -
2	5	0101 -
	9	1001 -
	10	1010 -
3	7	0111 -
	11	1011 -
	14	1110 -
4	15	1111 -

Step 3: 2-cell Grouping.

2-cell	Binary equivalent.
(8, 9)	100 - -
(8, 10)	10 - 0 -
(5, 7)	01 - 1 - → (A)
(9, 11)	10 - 1 -
(10, 11)	101 - -
(10, 14)	1 - 10 -
(7, 15)	- 111 - → (B)
(11, 15)	1 - 11 -
(14, 15)	111 - -

Step 4: 4-cell Grouping

4-cell	Binary equivalent.
(8, 9, 10, 11)	10 - -
(8, 10, 9, 11)	10 - -
(10, 11, 14, 15)	1 - 1 -
(10, 14, 11, 15)	1 - 1 -

Step 5: Remove Redundant.

4-cell	Binary equivalent
(8, 9, 10, 11)	10 - -
(10, 11, 14, 15)	1 - 1 -

Prime implicants are,

(5, 7)	ABCD 01-1	A'B'D
(7, 15)	-111	BCD
(8, 9, 10, 11)	10--	AB'
(10, 11, 14, 15)	1-1-	AC

Prime Implicant Chart:

	5	7	8	9	10	11	14	15
(*) (5, 7)	(*)	*						
(7, 15)		*						*
(*) (8, 9, 10, 11)			*	(*)	*	*		
(*) (10, 11, 14, 15)					*	*	(*)	*


$$SOP = A'B'D + AB' + AC$$

UNIT 2

13.Design a circuit that converts BCD code to Excess-3 code converter.


BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

 To find the corresponding digital circuit, we will use the K-Map technique for each of the Excess-3 code bits as output with all of the bits of the BCD number as input.



Corresponding minimized Boolean expressions for Excess-3 code bits –

The corresponding digital circuit-

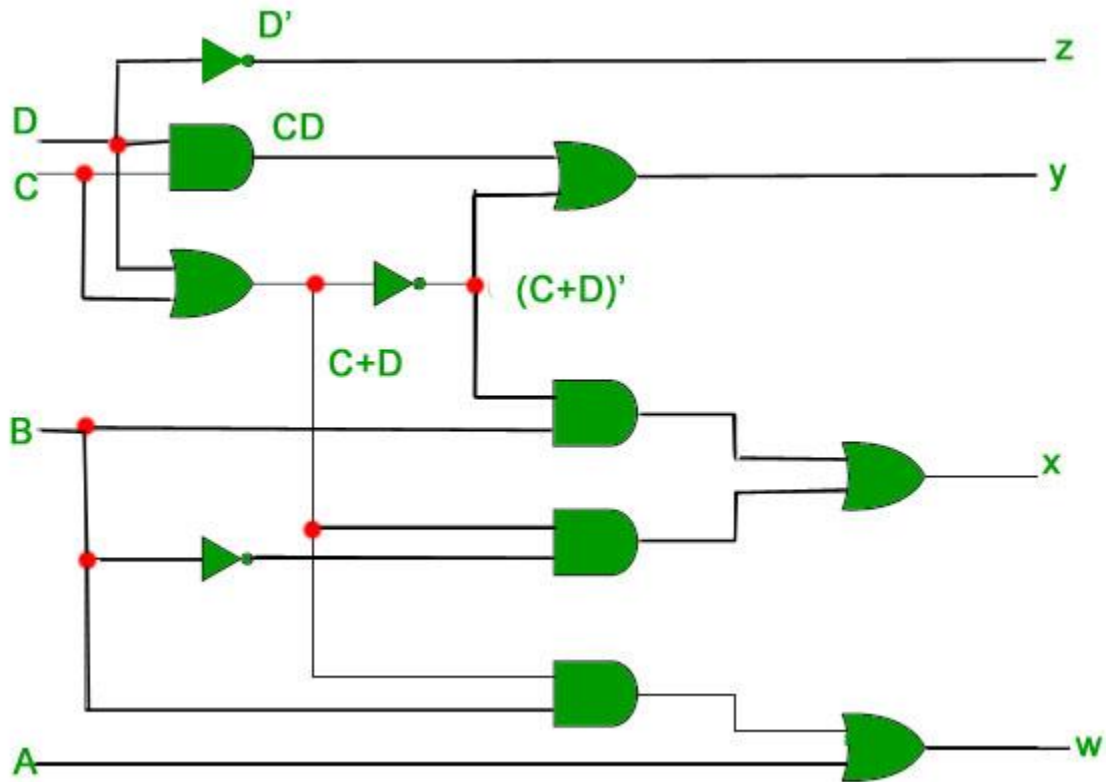

OR

14. Implement the switching function $F = \sum m(3, 6, 7, 8, 10, 12, 13, 14, 15)$ using an 8 input multiplexer.


In the given boolean expression, there are 4 variables. We should use $2^4 : 1 = 16 : 1$ multiplexer. But as per the question, it is to be implemented with $8 : 1$ mux.

For $8 : 1$ multiplexer, there should be 3 selection lines. So from the given 4 variables, the 3 least significant variables (B, C, D) are used as selection line inputs.

The 8 inputs are derived using the implementation table shown below

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
\bar{A}	0	1	2	(3)	4	5	(6)	(7)
A	(8)	9	(10)	11	(12)	(13)	(14)	(15)
	A	0	A	\bar{A}	A	A	1	1

From the derived input 8:1 multiplexer, can be drawn as below.

 

UNIT 3

15.A sequential circuit has two flip flops A and B,two inputs x and y and one output z.the flip flop input equations and circuit output equations are:

$$J_A = Bx + B'y'$$

$$K_A = B'xy'$$


$$J_B = A'x$$

$$K_B = A + xy'$$

$$Z = Ax'y' + Bx'y'$$

Draw the logic diagram and tabulate the state table.

State diagram:

 

STATE TABLE:

Present state		Input		Flip-Flop Inputs				Next state		Output
A	B	x	y	$J_A = Bx + B'y'$	$K_A = B'xy'$	$J_B = A'x$	$K_B = A + xy'$	A(t+1)	B(t+1)	z
0	0	0	0	1	0	0	0	1	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	1	1	1	1	0
0	0	1	1	0	0	1	0	0	1	0


0	1	0	0	0	0	0	0	0	0	1
0	1	0	1	0	0	0	0	0	0	0
0	1	1	0	1	0	1	1	1	1	0
0	1	1	1	1	0	1	0	1	1	0
1	0	0	0	1	0	0	1	1	0	1
1	0	0	1	0	0	0	1	1	0	0
1	0	1	0	1	1	0	1	0	0	0
1	0	1	1	0	0	0	1	1	0	0
1	1	0	0	0	0	0	1	1	0	1
1	1	0	1	0	0	0	1	1	0	0
1	1	1	0	1	0	0	1	1	0	0
1	1	1	1	1	0	0	1	1	0	0







STATE EQUATION:

For A(t+1)					For B(t+1)				
AB \ xy	00	01	11	10	AB \ xy	00	01	11	10
00	1	0	0	1	00	0	0	1	1
01	0	0	1	1	01	0	0	1	1
11	1	1	1	1	11	0	0	0	0
10	1	1	1	0	10	0	0	0	0

$A(t+1) = Ax' + Ay + Bx + A'B'y'$
 $B(t+1) = A'x$

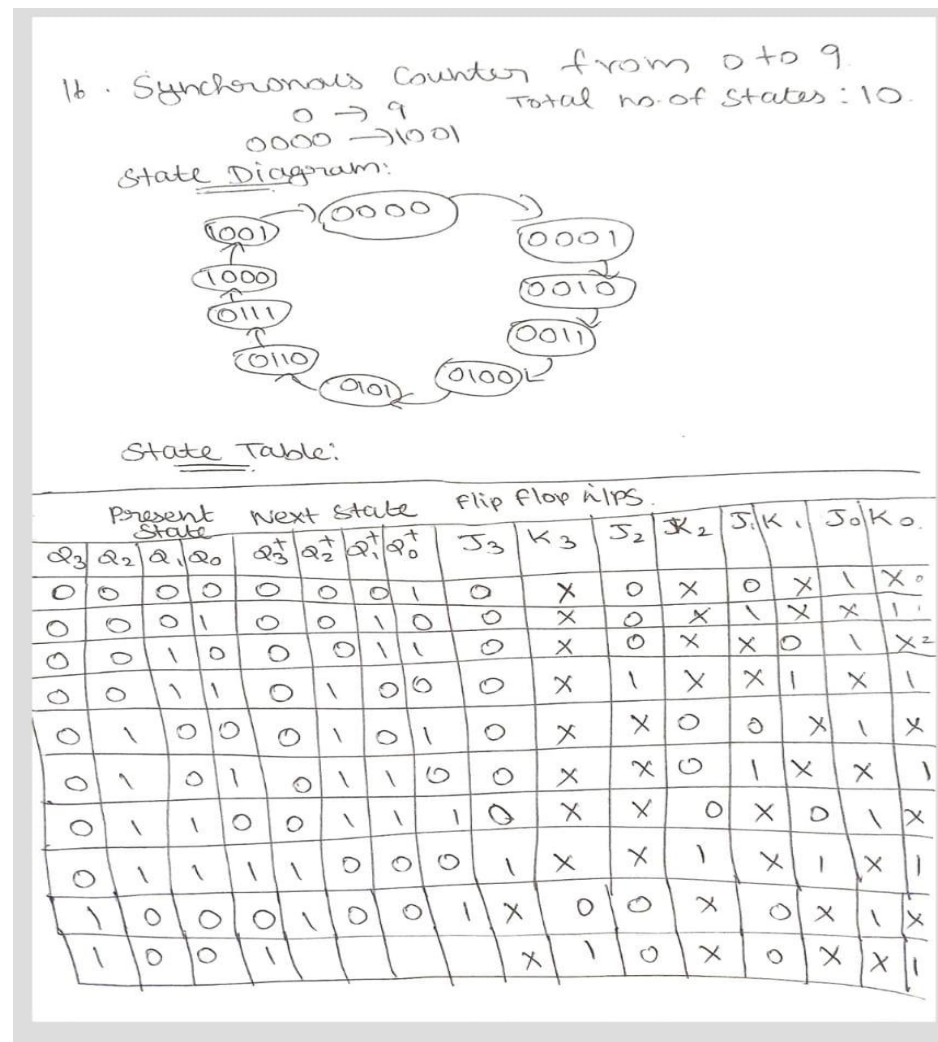
16. Design a BCD synchronous counter using JK flip flop.



      

$J_0 = \bar{Q}_1 + Q_1 \Rightarrow J_0 = 1$

 $K_0 = \bar{Q}_3 + Q_3 \Rightarrow K_0 = 1$



BCD counter using JK-FF.

UNIT 4

17. combinational logic is defined by the functions $F = \Sigma(3, 4, 5, 7, 10, 14, 15)$ AND $\Sigma(1, 5, 7, 11, 15)$. IMPLEMENT the circuit using a programmable logic array with 4 inputs, 6 product terms and 2 outputs.

Solution:

$$F_1 = \Sigma m(3, 4, 5, 7, 10, 14, 15)$$

$$F_2 = \Sigma m(1, 5, 7, 11, 15)$$

K-map for F_1 :

ab \ cd	00	01	11	10
00			1	
01	1	1	1	
11			1	1
10				1

$$F_1 = a'bc' + a'cd + acd' + bcd$$

K-map for F_2 :


ab \ cd	00	01	11	10
00		1		
01		1	1	
11			1	
10			1	

$$F_2 = A'C'D + BCD + ACD$$

PLA Table.

Product Term	a	b	c	d	F ₁	F ₂
$a'bc'$	0	1	0	-	1	-
$a'cd$	0	-	1	1	1	-
bcd	-	1	1	1	1	1
$a'c'd$	0	-	0	1	-	1
acd	1	-	1	1	-	1
$a'cd'$	1	-	1	0	1	-

Logic Diagram.

 

OR


18. Tabulate the PAL programming table for the four Boolean functions listed below.

$$A(x,y,z) = \Sigma(1,2,4,6)$$

$$B(x,y,z) = \Sigma(0,1,6,7)$$

$$C(x,y,z) = \Sigma(2,6)$$

 
$$D(x,y,z) = \Sigma(1,2,3,5,7) \text{ simplify using K-map.}$$



PAL Program Table

	Product Terms	AND inputs			outputs
		x	y	z	
1	$x̄z$	1	-	0	$A = x̄z + x̄yz + yz̄$
2	$x̄ȳz$	0	0	1	
3	$yz̄$	-	1	0	
4	$x̄ȳ$	0	0	-	$B = x̄ȳ + xy$
5	xy	1	1	-	
6	$yz̄$	-	1	0	$C = yz̄$
7	z	-	-	1	$D = z + x̄y$
8	$x̄y$	0	1	-	

Logic Diagram:-

 

UNIT 5

19. Interpret a Verilog HDL code to perform read and write operation of memory.

HDL Example 7.1


```
// Read and write operations of memory
// Memory size is 64 words of four bits each.

module memory (Enable, ReadWrite, Address, DataIn, DataOut);
  input  Enable, ReadWrite;
  input  [3: 0] DataIn;
  input  [5: 0] Address;
  output [3: 0] DataOut;
  reg [3: 0] DataOut;
  reg [3: 0] Mem [0: 63];           // 64 x 4 memory
  always @ (Enable or ReadWrite)
    if (Enable)
      if (ReadWrite) DataOut = Mem [Address]; // Read
      else Mem [Address] = DataIn;           // Write
      else DataOut = 4'bz;                   // High impedance state
endmodule
```


OR

 20. Design Verilog module for an edge triggered D Flip flop in the data flow model.

D Flip-Flop is a fundamental component in digital logic circuits. Verilog code for D Flip Flop is presented in this project. There are two types of D Flip-Flops being implemented which are Rising-Edge D Flip Flop and Falling-Edge D Flip Flop.



Rising-Edge D Flip-Flop

 

Falling-Edge D Flip-Flop

```
module RisingEdge_DFliPFlop(D,clk,Q);
  input D; // Data input
  input clk; // clock input
  output Q; // output Q
```

```
always @(posedge clk)
begin
  Q <= D;
end
endmodule
```

```
module FallingEdge_DFlop(D,clk,Q);
input D; // Data input
input clk; // clock input
output reg Q; // output Q
always @(negedge clk)
begin
  Q <= D;
end
endmodule
```